
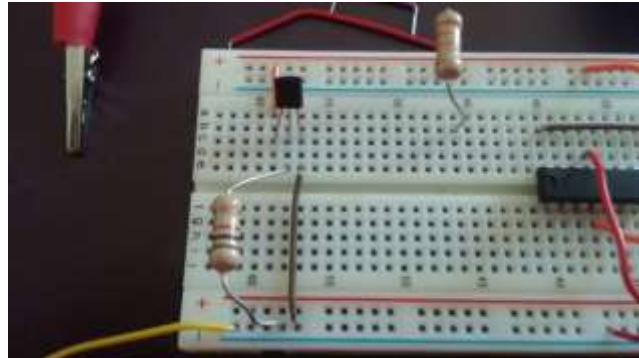


Designing a Thermostat Worksheet

Most of us have a thermostat in our homes to control heating and cooling systems of our home. These important devices help us save energy by automatically turning off energy intensive equipment when not needed. How do these devices work? In this activity, we'll use an electronic sensor and Ohm's Law to design and build a thermostat.

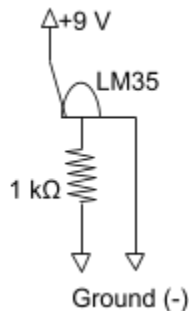Part 1: How can you measure temperature electronically?

- Obtain a breadboard, jumper wires, 9 V battery (with battery connectors), and an LM35 Temperature Sensor chip. Build the circuit shown to the right.



To save energy, connect the battery only when taking measurements.

- With a multimeter, measure the voltage across the 1 kΩ resistor. You should get a positive value around 0.23 V. Rub your hands together and touch the top of the LM35 sensor. What happens to the voltage reading?

- Now let's calibrate the sensor by developing an equation we can use to convert from voltage to temperature in Celsius (°C). Hint: Rub your hands together to heat them up.

- Complete table to the right, measuring the room and your palm with a thermometer and the circuit you just built.

| | Voltage (V) | Temp (°C) |
|------|-------------|-----------|
| Room | | |
| Palm | | |

- Assume a linear relationship between voltage across the 1 kΩ resistor and temperature. Using your data, develop an equation to determine voltage across the 1 kΩ resistor in terms of temperature (°C).

| | |
|---|--|
| <p>i. $V_2 = I/R_2$ ii. $V_2 = IR_2$</p> | <p>iii. $V_2 = R_2/I$ iv. $V_2 = I + R_2$</p> |
|---|--|


6. With the relationships between current and voltage from (5), you can determine an equation to quantify the value of R_1 .
- a. Substitute the equation for (5c) into the equation for (5d).

| | |
|--|--|
| | |
|--|--|

- b. Solve the equation you just found for R_1 .
- c. Plug in the known values ($V_{Bat} = 9\text{ V}$, $R_2 = 1\text{ k}\Omega$, V_2 set point) into your equation and calculate the value needed for R_1 .

| | |
|--|--|
| | |
|--|--|

7. Obtain the necessary resistor (s) and build your divider as shown to the right. Use the multimeter to ensure you obtained the desired value for V_2 . Is it correct?

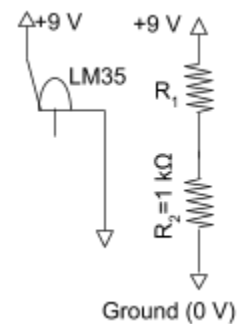

Part 3: Does the light turn on when it is supposed to?

8. Now you can connect your LM35 sensor and voltage divider to an operational amplifier (LM324). Add the LM324, $2\text{ k}\Omega$ resistor, light emitting diode (LED) and connections shown to the right to your breadboard. NOTE: The bridges show where wires are NOT connected.

Name: _____ Date: _____ Class: _____

14. Redesign your thermostat for the “nobody’s home” situation. Show calculations below and build it. Does it work?

| | |
|--|--|
| | |
|--|--|

Part 5: Can you use the circuit for a heating circuit?

15. In a heating circuit, the heater turns on when the temperature gets too low. Adjust the circuit so it will work for heating. Note how you changed the circuit and show calculations below. Obtain a bag of ice or cool object and see if it works.

Need to do the following:

1. Adjust R_1 so the set point is BELOW room temperature (maybe 19°C).
2. Switch connections to Pin 13 and Pin 12. Now the LM35 should be connected to PIN 13 and V_2 should be connected to PIN 12. Initially, room temperature (LM35) will be higher than the set point. Then the temperature of the LM35 goes below the set point it will turn on the circuit since the voltage to Pin 12 will be greater than Pin 13.

Part 6: Can “on” and “off” be at different temperatures?

16. Why would you want “on” and “off” to be set at different temperatures?

17. Continuing to use the heating circuit, complete the table below.

| State | Temperature (°C) | LM35 Voltage (V) |
|----------------------------------|------------------|------------------|
| Turns On (lower limit) | | |
| Turns Off (upper limit) | | |

Name: _____ Date: _____ Class: _____

| | |
|--|--|
| | |
| | |

24. Now, put in the appropriate R_4 and test it. Did it behave appropriately? Explain.