

Team Name: _____ Date: _____

Completing the Circuit Worksheet




1. In the space below, draw two ways to light the bulb. Use the symbols below.


2. What do you have to do to get the bulb to light up?

3. Draw two ways to connect the bulb, battery and wire so the bulb does not light. Use the symbols below.

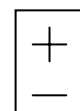4. Choose the right answer to complete the sentence:
There will be an electric current in _____ circuit.
A. an open
B. a closed
C. a big
D. a long



Battery

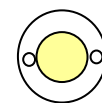

Light bulb



Wire