

Name: _____ Date: _____

In a Row Math Worksheet



1. Draw a circuit diagram for a circuit that has one battery and two light bulbs connected in series.
2. For the above circuit, one bulb has a resistance of 2Ω and a second bulb has a resistance of 3Ω . The total resistance for two bulbs in series is equal to the sum of their resistances.

Use this equation to find the total resistance of the circuit: $R_{\text{total}} = R_1 + R_2$
3. For a circuit that has one battery and two light bulbs connected in series, one bulb has a resistance of 1Ω , and the total resistance of the circuit is 6Ω . What is the resistance of the second light bulb?
4. If a circuit has two 1.5 V batteries in series, what is the voltage across the two batteries?
5. If a circuit has two 1.5 V batteries in series and one 3Ω light bulb, what is the current in the circuit?

Use the Ohm's law equation: $I = \frac{V}{R}$