


Name:


Date:


Class:

Flashlight Circuit Worksheet

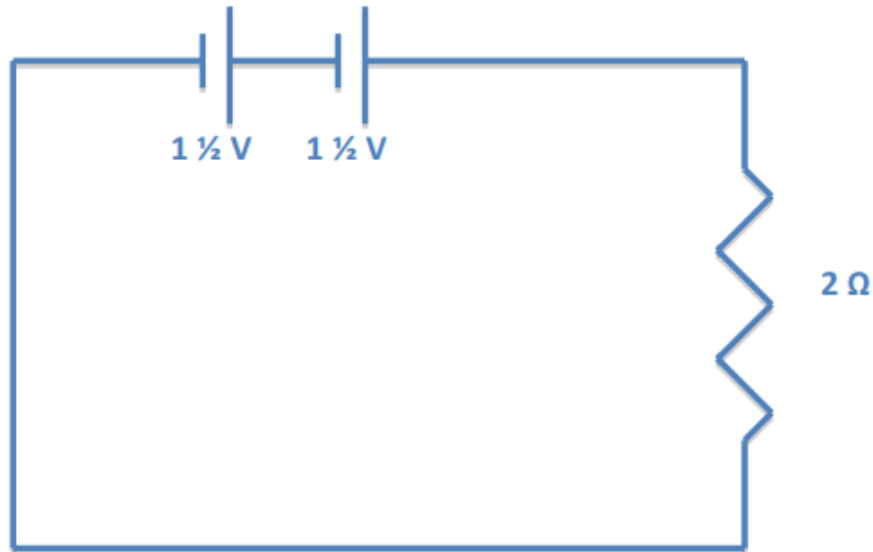Engineers would draw the flashlight circuit as shown below:



1. What do you think the symbol  represents?

2. What do you think the symbol  represents?

3. How many total volts [V] are in the circuit?