
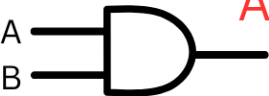


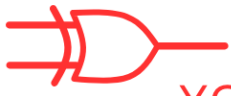




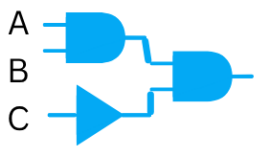


Name:

Date:

Class:

Logic Gates I Worksheet **Answer Key**

 <p>AND</p> <p>Label the gate and then draft a truth table for its outcomes.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table> <p><i>Group Example</i></p>	A	B	Output	0	0	0	0	1	0	1	0	0	1	1	1	 <p>XOR</p> <p>Create an XOR gate and then draft its truth table.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table> <p><i>Group Example</i></p>	A	B	Output	0	0	0	0	1	1	1	0	1	1	1	0
A	B	Output																													
0	0	0																													
0	1	0																													
1	0	0																													
1	1	1																													
A	B	Output																													
0	0	0																													
0	1	1																													
1	0	1																													
1	1	0																													
 <p>NAND</p> <p>Look at the truth table. Draw a logic gate that represents it.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table> <p><i>Group Example</i></p>	A	B	Output	0	0	1	0	1	1	1	0	1	1	1	0	 <p>OR</p> <p>Label the gate and then draft a truth table for its outcomes.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Output	0	0	0	0	1	1	1	0	1	1	1	1
A	B	Output																													
0	0	1																													
0	1	1																													
1	0	1																													
1	1	0																													
A	B	Output																													
0	0	0																													
0	1	1																													
1	0	1																													
1	1	1																													
 <p>AND</p> <p>Create an AND gate and then draft its truth table.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Output	0	0	0	0	1	0	1	0	0	1	1	1	 <p>AND</p> <p>Look at the truth table. Draw a logic gate that represents it.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Output	0	0	0	0	1	0	1	0	0	1	1	1
A	B	Output																													
0	0	0																													
0	1	0																													
1	0	0																													
1	1	1																													
A	B	Output																													
0	0	0																													
0	1	0																													
1	0	0																													
1	1	1																													
 <p>NOR</p> <p>Create an NOR gate and then draft its truth table.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Output	0	0	1	0	1	0	1	0	0	1	1	0	 <p>NAND</p> <p>Look at the truth table. Draw a logic gate that represents it.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Output	0	0	1	0	1	1	1	0	1	1	1	0
A	B	Output																													
0	0	1																													
0	1	0																													
1	0	0																													
1	1	0																													
A	B	Output																													
0	0	1																													
0	1	1																													
1	0	1																													
1	1	0																													
 <p>NOR</p> <p>Label the gate and then draft a truth table for its outcomes.</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Output	0	0	1	0	1	0	1	0	0	1	1	0	 <p>Challenge Problem!</p> <p>Create a truth table for this series of Logic Gates.</p> <p>Refer to Logic Gates II for the truth table!</p>															
A	B	Output																													
0	0	1																													
0	1	0																													
1	0	0																													
1	1	0																													

Name:

Date:

Class:

**AND**

Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

Group Example**XOR**

Create an XOR gate and then draft its truth table.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Group Example**NAND**

Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

Group Example**NAND**


Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

**OR**

Create an OR gate and then draft its truth table.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

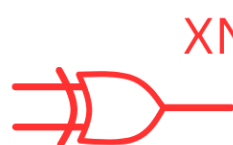**XNOR**

Look at the truth table. Draw a logic gate that represents it.


A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

NOR

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0



Label the gate and then draft a truth table for its outcomes.

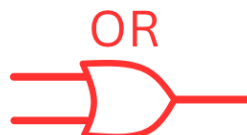**OR**


Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

**AND**

Create an AND gate and then draft its truth table.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

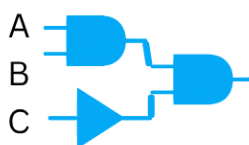

Refer to Logic Gates II for the truth table!

★ **Challenge Problem!**


Create a truth table for this series of Logic Gates.

Name:

Date:

Class:

AND

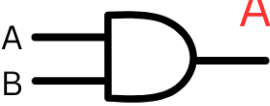


Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

Group Example

XOR

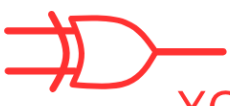


Create an XOR gate and then draft its truth table.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Group Example

NAND

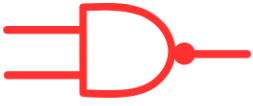


Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

Group Example


XOR

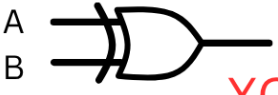

Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0


NAND

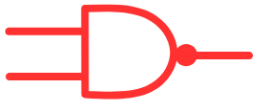

Create an NAND gate and then draft its truth table.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0


XNOR

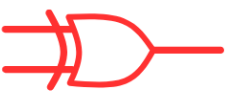

Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1


NOT

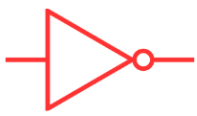

Create an NOT gate and then draft its truth table.

Input	Output
0	1
1	0


AND

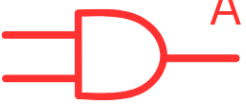

Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1


NOR



Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Challenge Problem!

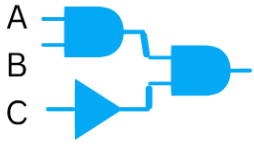

Refer to Logic Gates II for the truth table!


Create a truth table for this series of Logic Gates.

Name:

Date:

Class:

AND

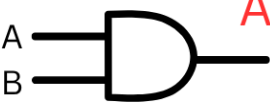


Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

Group Example

XOR

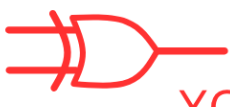


Create an XOR gate and then draft its truth table.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Group Example

NAND




Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

Group Example


NOR



Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0


AND



Create an AND gate and then draft its truth table.

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1


NOR



Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0


OR



Create an OR gate and then draft its truth table.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1


XNOR



Look at the truth table. Draw a logic gate that represents it.

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0


NAND



Label the gate and then draft a truth table for its outcomes.

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

Challenge Problem!

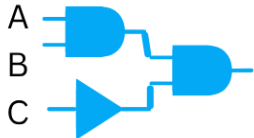

Refer to Logic Gates II for the truth table!

Create a truth table for this series of Logic Gates.