

Name:

Date:

Class:

## Logic Gates II Worksheet

A Logic circuit has two inputs being X and Y. Fill in all the possible combinations.

X	Y

A Logic circuit has three inputs being X, Y, and Z. Fill in all the possible combinations.

X	Y	Z

In this activity, you will create truth tables for logic gates that have three inputs. Make sure to reference your notes if you forget which symbols represent what gates!

