

Name:

Date:

Class:

LOGIC GATES AND TRUTH TABLES

Buffer



INPUT	OUTPUT
1	1
0	0

Does not change the input. Same output as input

NOT



INPUT	OUTPUT
1	0
0	1

output is the opposite of the input

AND



A	B	OUTPUT
1	1	1
1	0	0
0	1	0
0	0	0

output is 1 only if every input is 1

NAND



A	B	OUTPUT
1	1	0
1	0	1
0	1	1
0	0	1

output is 0 only if every input is 1

OR



A	B	OUTPUT
1	1	1
1	0	1
0	1	1
0	0	0

output is 1 if any input is 1

NOR



A	B	OUTPUT
1	1	0
1	0	0
0	1	0
0	0	1

output is 1 only if every input is 0

XOR



A	B	OUTPUT
1	1	0
1	0	1
0	1	1
0	0	0

output is 1 if inputs differ

XNOR



A	B	OUTPUT
1	1	1
1	0	0
0	1	0
0	0	1

output is 1 if inputs match