

Name:

Date:

Class:

LOGIC GATES AND TRUTH TABLES

Buffer



INPUT	OUTPUT
1	1
0	0

Does not change the input. Same output as input



INPUT	OUTPUT



A	B	INPUT	OUTPUT




A	B	INPUT	OUTPUT



A	B	INPUT	OUTPUT



A	B	INPUT	OUTPUT

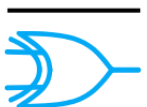

A	B	INPUT	OUTPUT



A	B	INPUT	OUTPUT